

Supplementary Problems (S-):

12. You are given three resistors: $3\ \Omega$, $6\ \Omega$, and $12\ \Omega$. (a) Draw a diagram showing how to connect the resistors so that you get the smallest effective resistance, and calculate that effective resistance. (b) Is your connection above purely parallel, purely series, or a combination? (c) Draw a second diagram showing how to connect the resistors so that you get the largest effective resistance, and calculate that effective resistance. (d) Draw a third diagram showing how to connect the resistors so that you get some value between $6\ \Omega$ and $12\ \Omega$ for the effective resistance, and calculate that effective resistance.

Answers to Supplementary Problems:

12. a) $R_{\text{eff}} = 1.714\ \Omega$; b) purely parallel; c) $R_{\text{eff}} = 21\ \Omega$.